

# DVLSI – PROJECT – 1

NAME – NAGABHUSHAN DESHPANDE

SRN – PES1UG21EC155

SEC – C

## INCLUDES –

1)SCHEMATIC AND LAYOUTS OF NAND GATE ,  
XOR , FULLADDER .

2)TRANSIENT ANALYSIS, OUTPUTWAVEFORM,  
POWER DISCIPATION , DELAY OF ALL 3 SCHEMATICS.

3)DRC , LVS , AREA OF NAND , XOR , FULLADDER . AND  
PEX OF FULLADDER.

## **AIM –**

### **IMPLEMENTING XOR AND FULL ADDER USING NAND GATES**

To find delay , power dissipation .

## **THEORY-**

A two input NAND gate can be constructed by using 4 transistors ,which are in series in the n-block and parallel in p-block.

This NAND can be used to construct a two input XOR gate using 4 NAND gates.

A one-bit FULL ADDER can be constructed with a total of 9 NAND gates.

Expression for NAND:  $Y = \overline{AB}$


Expression for XOR:  $Y = A\overline{B} + \overline{A}B$

Expressions for Full adder:  $S = A \oplus B \oplus C$


$C_{out} = AB + BC + CA$

## STEPS –

### 1) MAKE SCHEMATIC OF NAND GATE

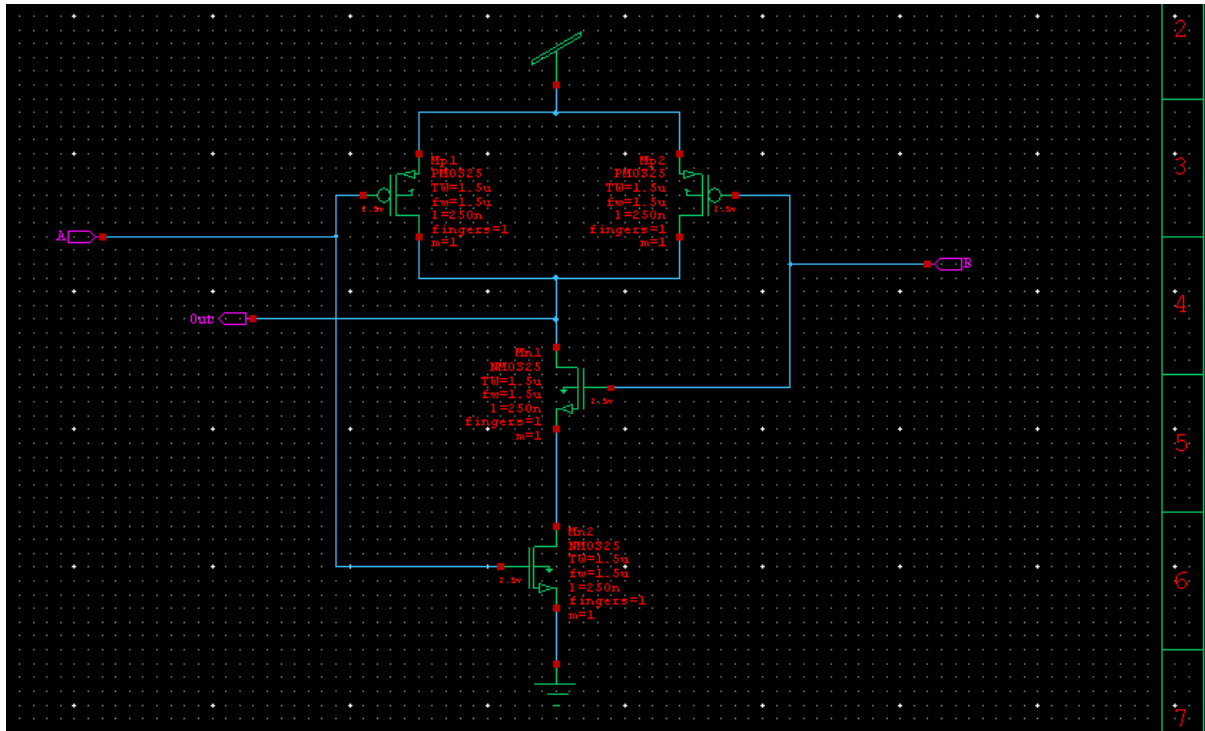

 And create nand symbol to get the out put waveform.



Power Results:

Average power consumed ->  $4.107428 \times 10^{-5}$  watts

Max power  $3.581262 \times 10^{-3}$  at time  $2.72522 \times 10^{-9}$

Min power  $4.885665 \times 10^{-11}$  at time 0


Delay Results:

B to Out = 24.7914n


A to Out = 208.5553p

2) Using the nand symbol , construct XOR gate .

Schematic of XOR.

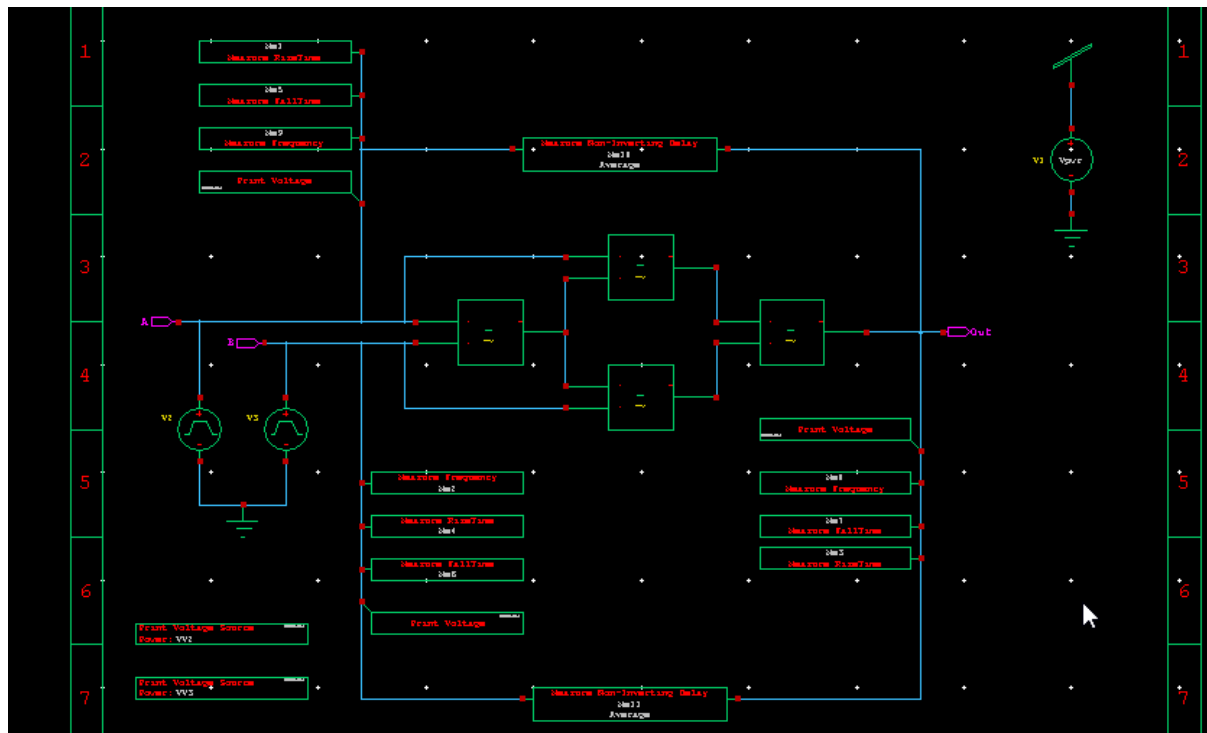

 Run the schematic to get output waveforms.



The XOR truth table can be verified from the waveform.

#### Power Results

vv1 from time 0 to 1e-06

Average power consumed -> 1.197393e-04 watts

Max power 1.402281e-02 at time 3.06719e-09

Min power 1.961674e-09 at time 0

vv2 from time 0 to 1e-06

Average power consumed -> 7.588312e-07 watts

Max power 6.480234e-05 at time 8.04556e-07

Min power 0.000000e+00 at time 0

vv3 from time 0 to 1e-06

Average power consumed -> 2.556680e-07 watts

Max power 7.445739e-05 at time 8.03143e-07

Min power 0.000000e+00 at time 0

#### Measurement result summary

Me10	=	-49.8689n
Me11	=	-99.8689n
Me1	=	4.0000n
Me3	=	674.2205p
Me4	=	4.0000n
Me5	=	4.0000n
Me6	=	4.0000n
Me7	=	199.7845p
Me2<Hz>	=	2.5000MEG
Me8<Hz>	=	9.9648MEG
Me9<Hz>	=	5.0000MEG

The power dissipation of XOR gate is

0.1197 milli watts.


The delay of XOR gate is

49.8689 ns.

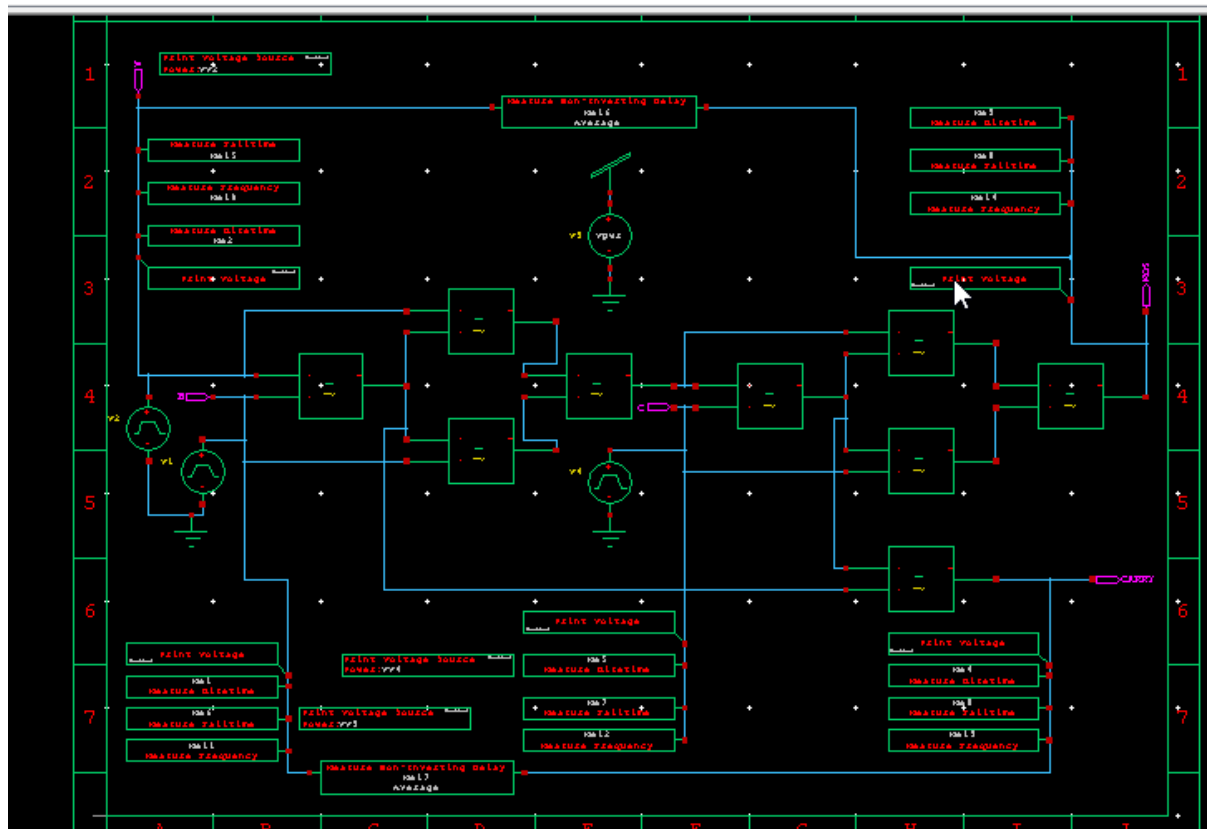
3) using nand gates , construct 1-bit-full adder

And obtain sum and carry outputs.

Schematic of Full adder using nand symbols.



# Output waveform -

 

Measurement result summary		
Me16	=	-50.1382n
Me17	=	-49.4926n
Me1	=	4.0000n
Me2	=	4.0000n
Me3	=	408.0130p
Me4	=	291.2530p
Me5	=	4.0000n
Me6	=	4.0000n
Me7	=	4.0000n
Me8	=	200.7266n
Me9	=	107.0119p
Me15	=	4.0000n
Me10<Hz>	=	5.0000MEG
Me11<Hz>	=	2.5000MEG
Me12<Hz>	=	1.6667MEG
Me13<Hz>	=	9.9144MEG
Me14<Hz>	=	733.2475MEG

---

#### Power Results

vv1 from time 0 to 1e-06  
Average power consumed -> 2.189020e-07 watts  
Max power 2.581627e-04 at time 1.03389e-07  
Min power 0.000000e+00 at time 0

vv2 from time 0 to 1e-06  
Average power consumed -> 1.412941e-07 watts  
Max power 6.901248e-05 at time 4.03241e-07  
Min power 0.000000e+00 at time 0

vv3 from time 0 to 1e-06  
Average power consumed -> 2.267197e-04 watts  
Max power 2.306721e-02 at time 6.02605e-07  
Min power 4.767377e-09 at time 0

vv4 from time 0 to 1e-06  
Average power consumed -> 2.697642e-08 watts  
Max power 6.892020e-04 at time 8.02362e-07  
Min power 0.000000e+00 at time 0

The power dissipation of Full adder is  
0.2267 milli watts.

The delay of full adder is  
50.1386 ns.



Observations –

Successfully noted the power dissipation and delay of nand , xor , fulladder .

Number of transistors used –


1 nand gate -> 4 transistors

1 XOR -> 4 nand gates -> 16 transistors


1 Fulladder -> 9 nand gates -> 36 transistors

# LAYOUT


## 1) NAND layout -

 


AREA – 130.2  $\mu\text{m}^2$

 


# NAND – DRC-

 


# NAND – LVS-

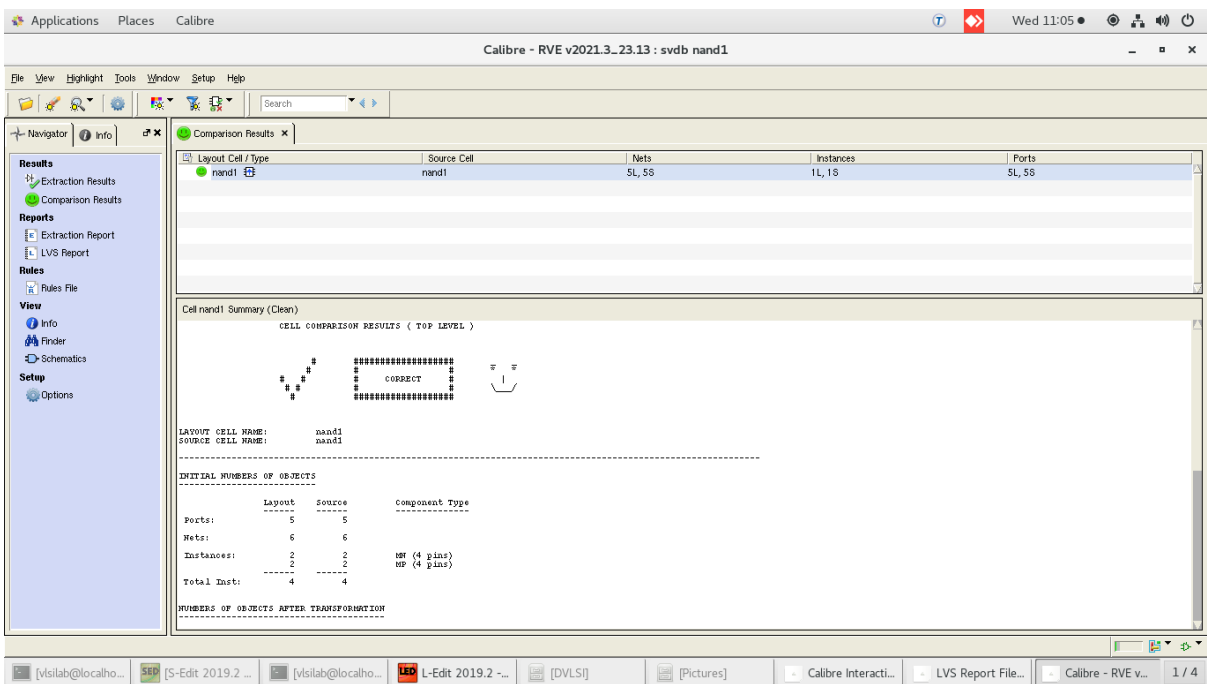


## XOR – LAYOUT-

 


## XOR – DRC –

 


# XOR – LVS –

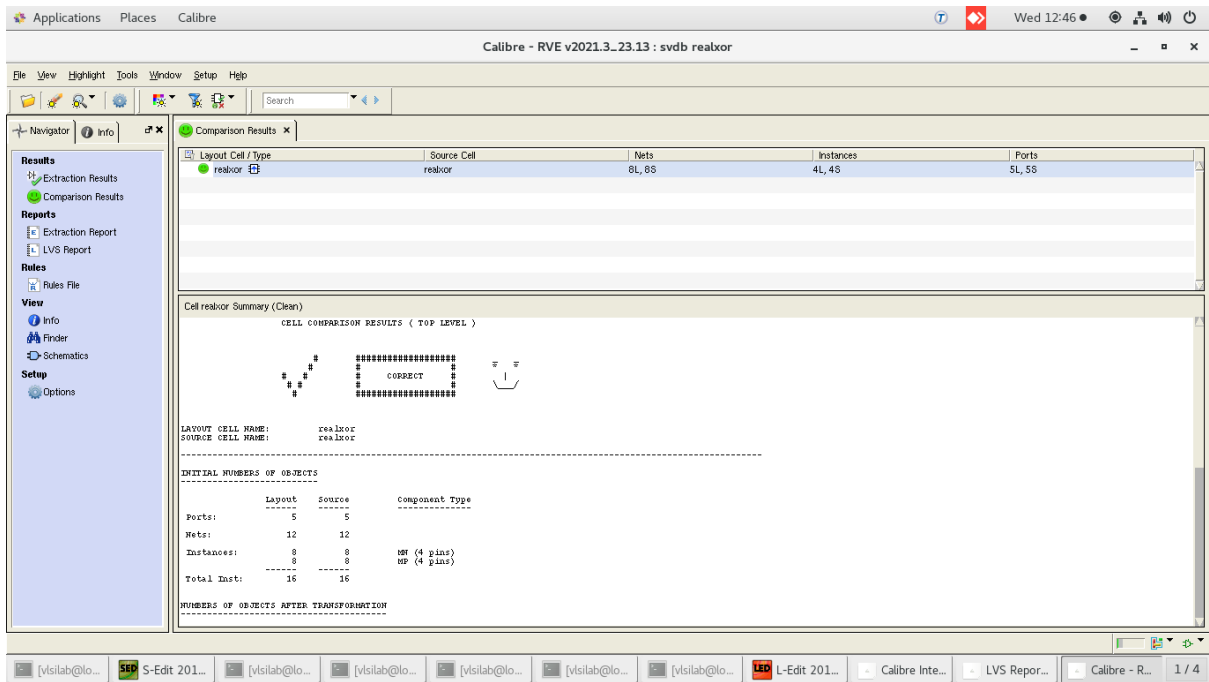


AREA – 1776.2  $\mu\text{m}^2$

 


## FULL ADDER layout –

 


## DRC –

 


LVS –

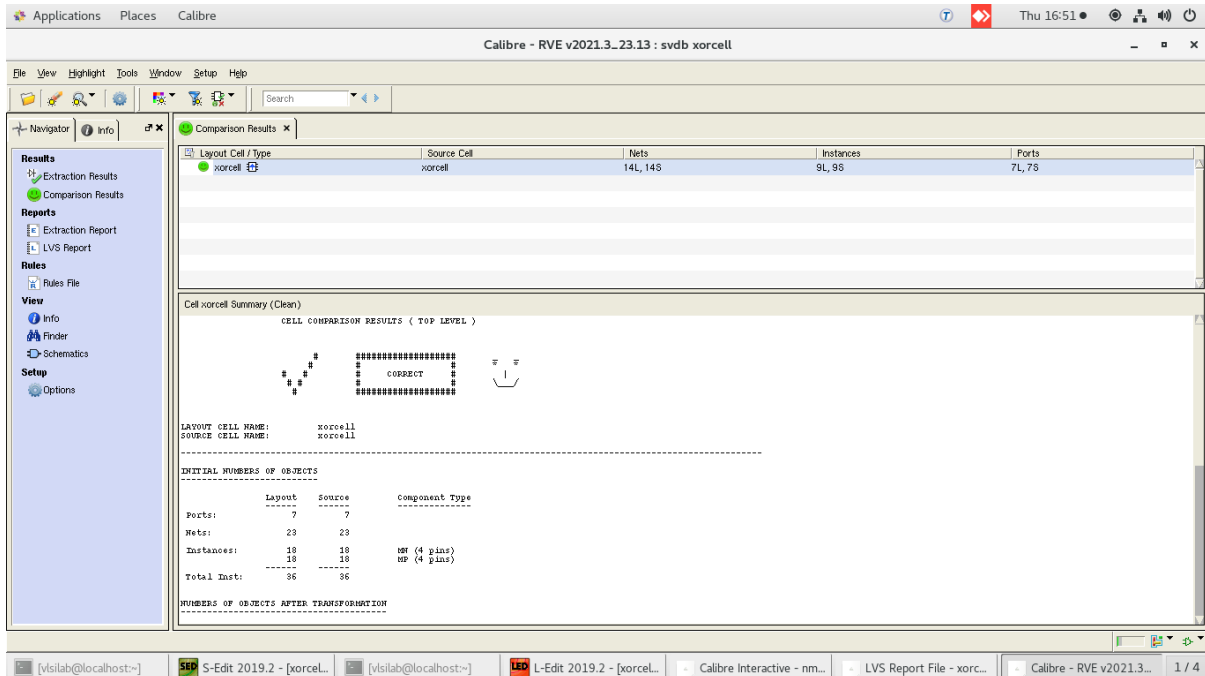

## PEX – netlist –

 

AREA – 6134.88  $\mu\text{m}^2$

 

Observation –

1) Full adder made using nand gates only , instead of using xor gates . Which will reduce the

Number of gates.

2) Area of layouts can be calculated by clicking 'T',

And calculating Length and Breadth